
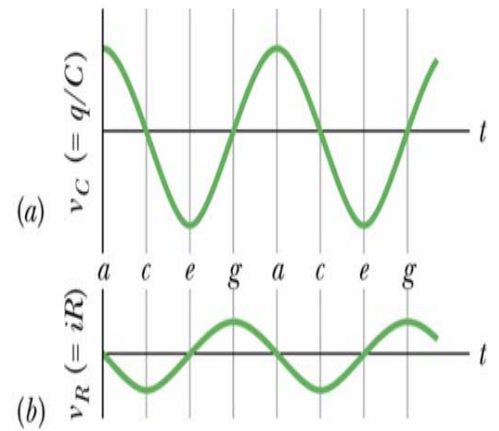


# Oscillazioni e onde

- Circuiti oscillanti
- Onde
- Onde elettromagnetiche


# Citcuito LC

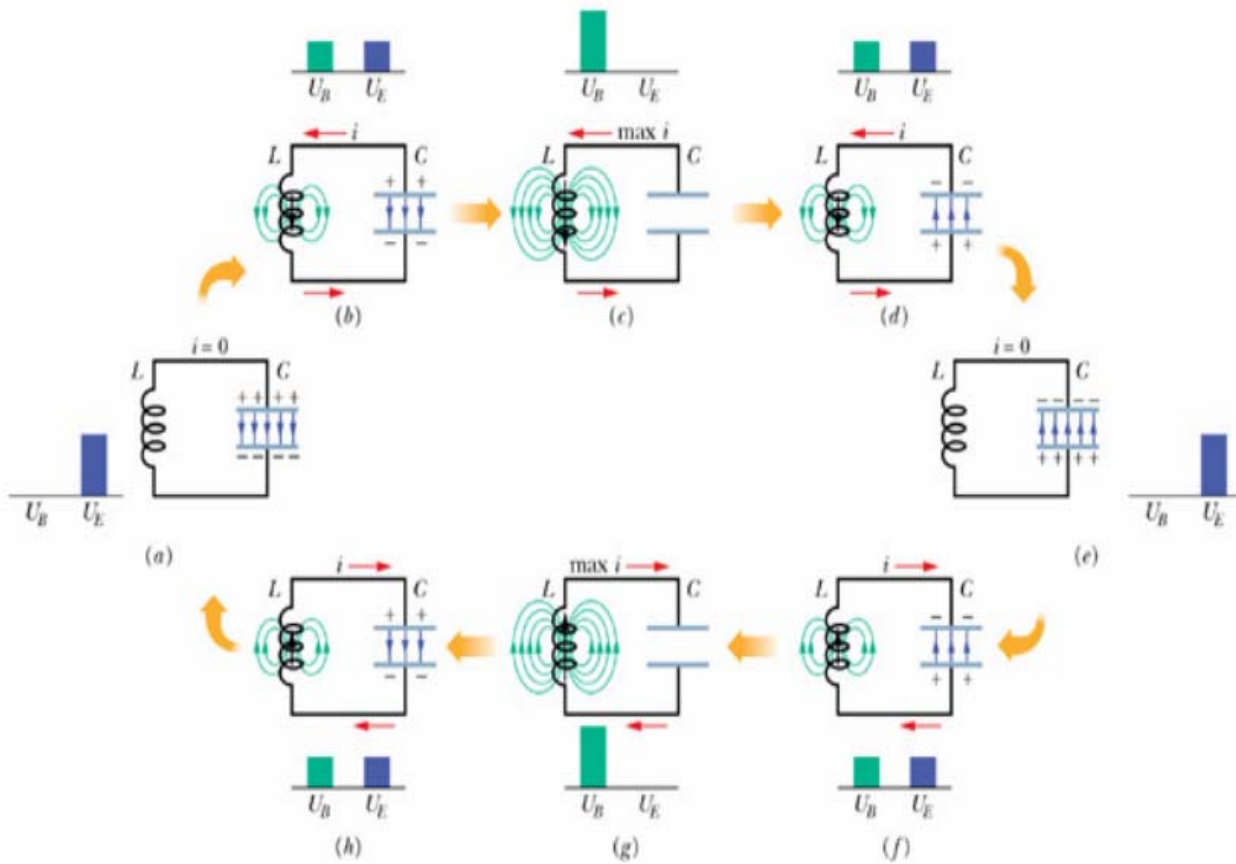
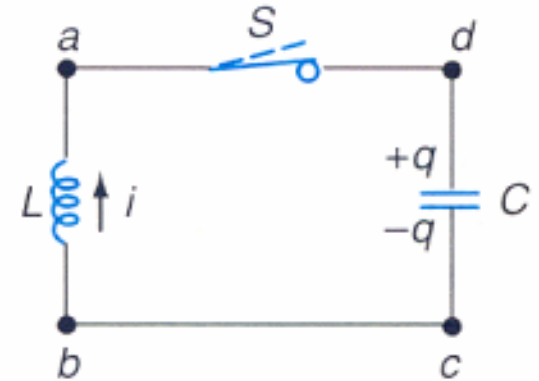
# Circuito LC

$$(V_b - V_a) + (V_c - V_b) + (V_d - V_c) + (V_a - V_d) = 0$$

$$L \frac{di}{dt} + \frac{q}{C} = 0 \quad i = \frac{dq}{dt} \quad \frac{di}{dt} = \frac{d^2 q}{dt^2}$$



$$\frac{d^2 q}{dt^2} = -\frac{1}{LC} q \quad \text{Eq. dell'oscillatore armonico}$$

$$q(t) = Q_m \cos(\omega_0 t + \varphi) \quad i(t) = \frac{dq}{dt} = -\omega_0 Q_m \sin(\omega_0 t + \varphi)$$

$$\frac{d^2 q}{dt^2} = -\omega_0^2 Q_m \cos(\omega_0 t + \varphi) \quad i_m = \omega_0 Q_m$$


$$-\omega_0^2 Q_m \cos(\omega_0 t + \varphi) = -\frac{1}{LC} Q_m \cos(\omega_0 t + \varphi)$$

# Circuito LC

$$\omega_0^2 = \frac{1}{LC} \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

condizioni iniziali  $q = Q_0, i = 0$
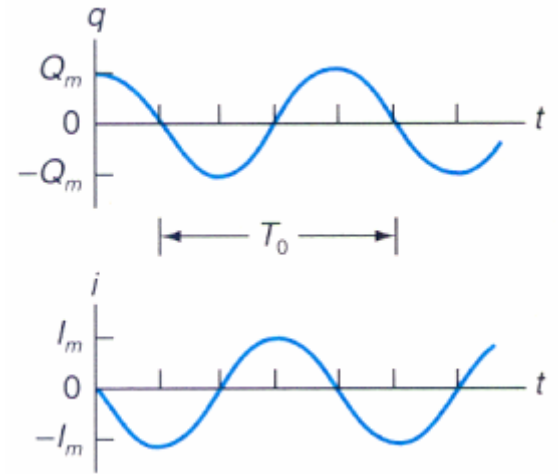
$$q = Q_0 \cos(\omega_0 t) \quad i = -i_m \sin(\omega_0 t)$$



$$U = U_E + U_B \quad U_E = \frac{q^2}{2C} = \frac{Q_m^2}{2C} \cos^2(\omega_0 t + \varphi)$$

Energia

$$U_B = \frac{1}{2} Li^2 = \frac{1}{2} Li_m^2 \sin^2(\omega_0 t + \varphi)$$

$$\frac{1}{2} Li_m^2 = \frac{1}{2} L(\omega_0 Q_m)^2 = \frac{1}{2} LQ_m^2 \frac{1}{LC} = \frac{Q_m^2}{2C}$$

$$U = \frac{1}{2} Li_m^2 = \frac{Q_m^2}{2C}$$

# Circuito RLC

$$f(t) = L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt.$$


$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = \frac{df}{dt}$$

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

$$i(t) = e^{kt}$$

$$e^{kt} \left[ Lk^2 + Rk + \frac{1}{C} \right] = 0.$$

$$Lk^2 + Rk + \frac{1}{C} = 0$$

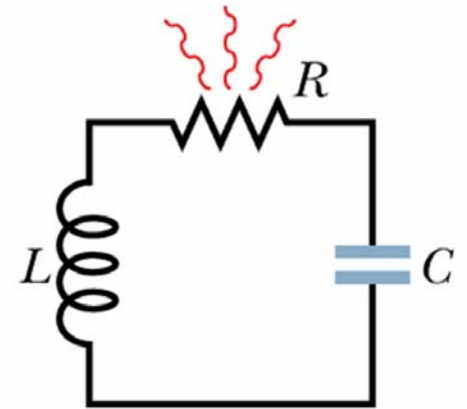

# Circuito RLC


$$k_1, k_2 = \frac{-R \pm \sqrt{R^2 - 4\frac{L}{C}}}{2L}$$

$$i(t) = A_1 e^{k_1 t} + A_2 e^{k_2 t}.$$

$$R^2 \cong 4\frac{L}{C}$$

$$R^2 > 4\frac{L}{C}$$

$$R^2 = 4\frac{L}{C}$$

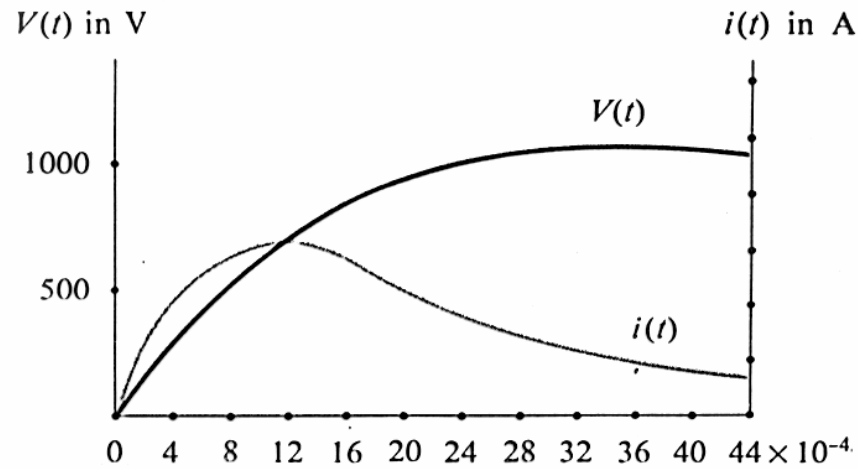


# Circuito RLC

$$R^2 < 4\frac{L}{C}$$

$$i(t) = e^{-\frac{R}{2L}t} (A_1 e^{i\omega_0 t} + A_2 e^{-i\omega_0 t})$$
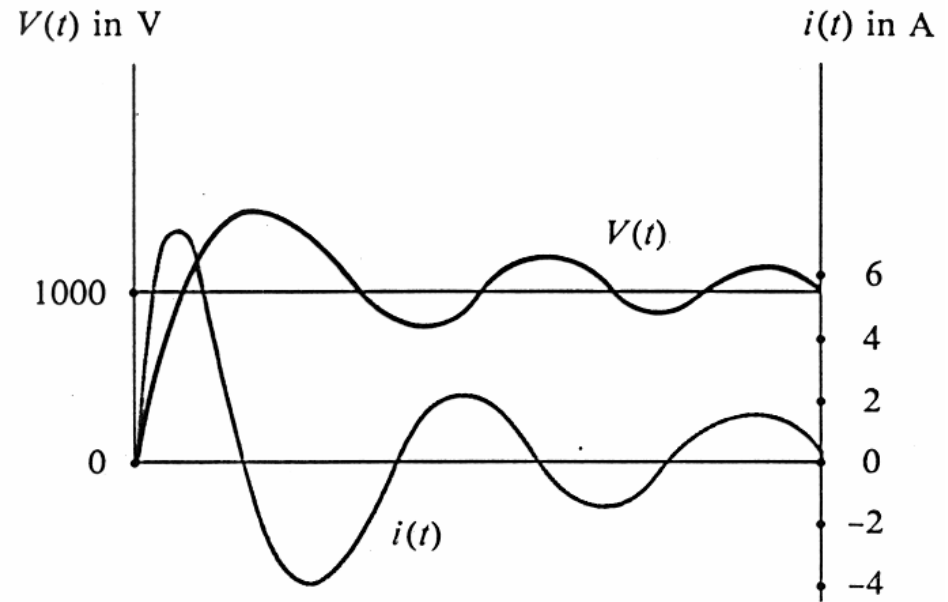
$$\nu_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$



$$\cos \theta = \frac{e^{i\theta} + e^{-i\theta}}{2}$$

# Circuito RLC

